

9 BASIC MULTIPLICATION SCHEMES

Chapter Goals

Study shift/add or bit-at-a-time multipliers and set the stage for faster methods and variations to be covered in Chapters 10-12

Chapter Highlights

Multiplication= multioperand addition
Hardware, firmware, software algorithms
Multiplying 2's-complement numbers
The special case of one constant operand

BASIC MULTIPLICATION SCHEMES: TOPICS

Topics in This Chapter

9.1 Shift/Add Multiplication Algorithms

9.3 Basic Hardware Multipliers

9.4 Multiplication of Signed Numbers

9.5 Multiplication by Constants

9.1 SHIFT/ADD MULTIPLICATION ALGORITHMS

Notation for our discussion of multiplication algorithms:

a	Multiplicand	$a_{k-1}a_{k-2} \dots a_1a_0$
x	Multiplier	$x_{k-1}x_{k-2} \dots x_1x_0$
p	Product ($a \times x$)	$p_{2k-1}p_{2k-2} \dots p_3p_2p_1p_0$

Initially, we assume unsigned operands


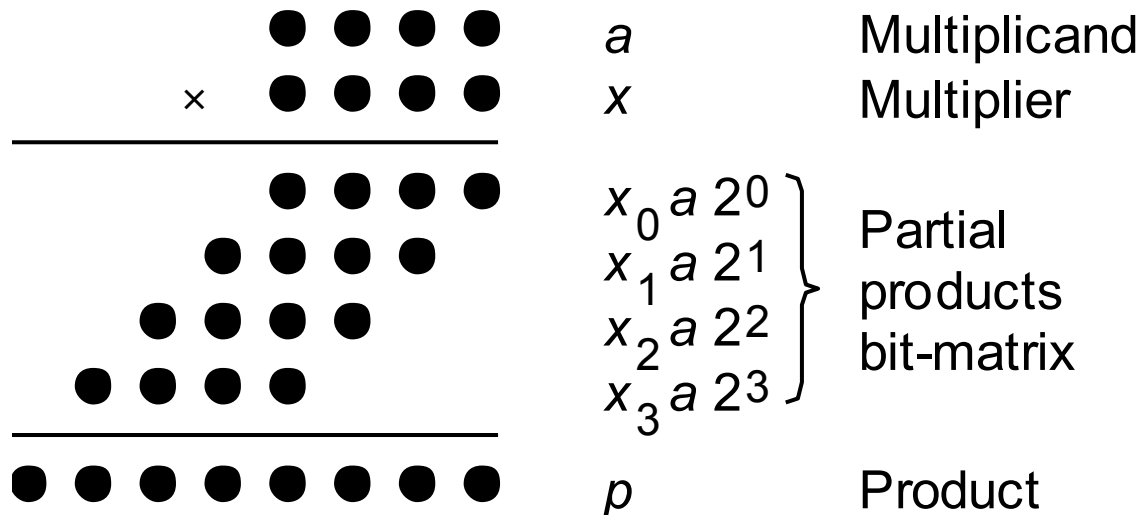


Fig. 9.1 Multiplication of two 4-bit unsigned binary numbers in dot notation.

MULTIPLICATION RECURRENCE

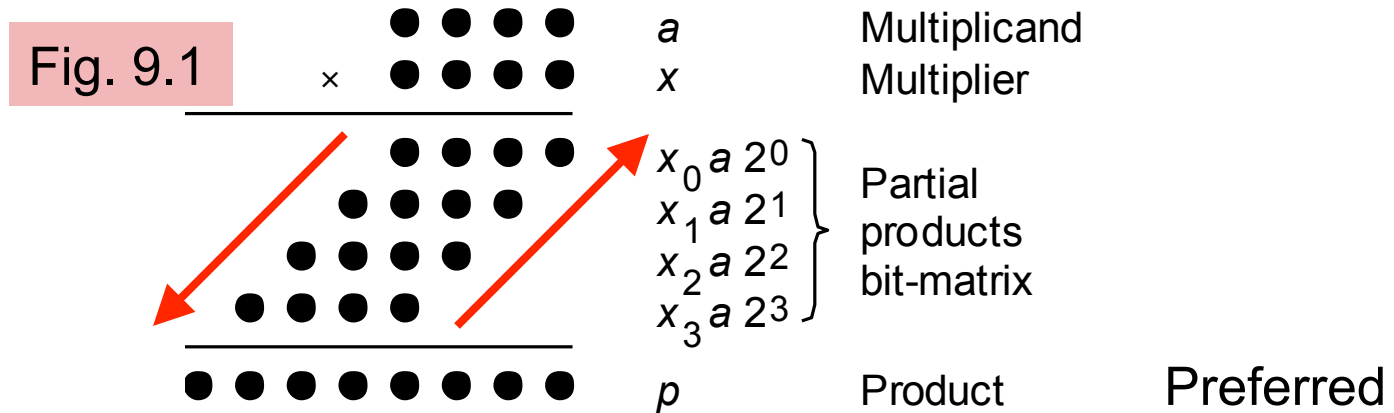

Multiplication with right shifts: top-to-bottom accumulation

$$p^{(j+1)} = (p^{(j)} + x_j a 2^k) 2^{-1} \quad \text{with} \quad p^{(0)} = 0 \quad \text{and}$$

|—add—|
|—shift right—|

Multiplication with left shifts: bottom-to-top accumulation

$$p^{(j+1)} = 2 p^{(j)} + x_{k-j-1} a \quad \text{with} \quad p^{(0)} = 0 \quad \text{and}$$

|shift|
|—add—|

EXAMPLES OF BASIC MULTIPLICATION

Right-shift algorithm

=====									
a	1	0	1	0	←	1	0	1	0
x						1	0	1	1
=====									
$p^{(0)}$	0	0	0	0					
$+x_0a$	1	0	1	0					
<hr/>									
$2p^{(1)}$	0	1	0	1	0				
$p^{(1)}$	0	1	0	1	0				
$+x_1a$	1	0	1	0					
<hr/>									
$2p^{(2)}$	0	1	1	1	1	0			
$p^{(2)}$	0	1	1	1	1	0			
$+x_2a$	0	0	0	0					
<hr/>									
$2p^{(3)}$	0	0	1	1	1	1	0		
$p^{(3)}$	0	0	1	1	1	1	0		
$+x_3a$	1	0	1	0					
<hr/>									
$2p^{(4)}$	0	1	1	0	1	1	1	0	
$p^{(4)}$	0	1	1	0	1	1	1	0	
=====									

Fig. 9.2
Examples
of
sequential
multipli-
cation with
right and
left shifts.

$$p^{(j+1)} = (p^{(j)} + x_j a 2^k) 2^{-1}$$

|——add——|
|——shift right——|

Check:

$$10 \times 11 = 110 = 64 + 32 + 8 + 4 + 2$$

EXAMPLES OF BASIC MULTIPLICATION (CONTINUED)

Fig. 9.2
Examples
of
sequential
multipli-
cation with
right and
left shifts.

$$p^{(j+1)} = 2p^{(j)} + x_{k-j-1}a$$

|shift|
|-----add-----|

Check:

$$10 \times 11 = 110 = 64 + 32 + 8 + 4 + 2$$

Left-shift algorithm

=====												
a									1	0	1	0
x									1	0	1	1
=====												
$p^{(0)}$									0	0	0	0
$2p^{(0)}$						0			0	0	0	0
$+x_3a$									1	0	1	0
=====												
$p^{(1)}$					0				1	0	1	0
$2p^{(1)}$				0	1				0	1	0	0
$+x_2a$									0	0	0	0
=====												
$p^{(2)}$					0	1			0	1	0	0
$2p^{(2)}$				0	1	0			1	0	0	0
$+x_1a$									1	0	1	0
=====												
$p^{(3)}$					0	1	1		0	0	1	0
$2p^{(3)}$				0	1	1	0		0	1	0	0
$+x_0a$									1	0	1	0
=====												
$p^{(4)}$				0	1	1	0		1	1	1	0
=====												

9.3 BASIC HARDWARE MULTIPLIERS

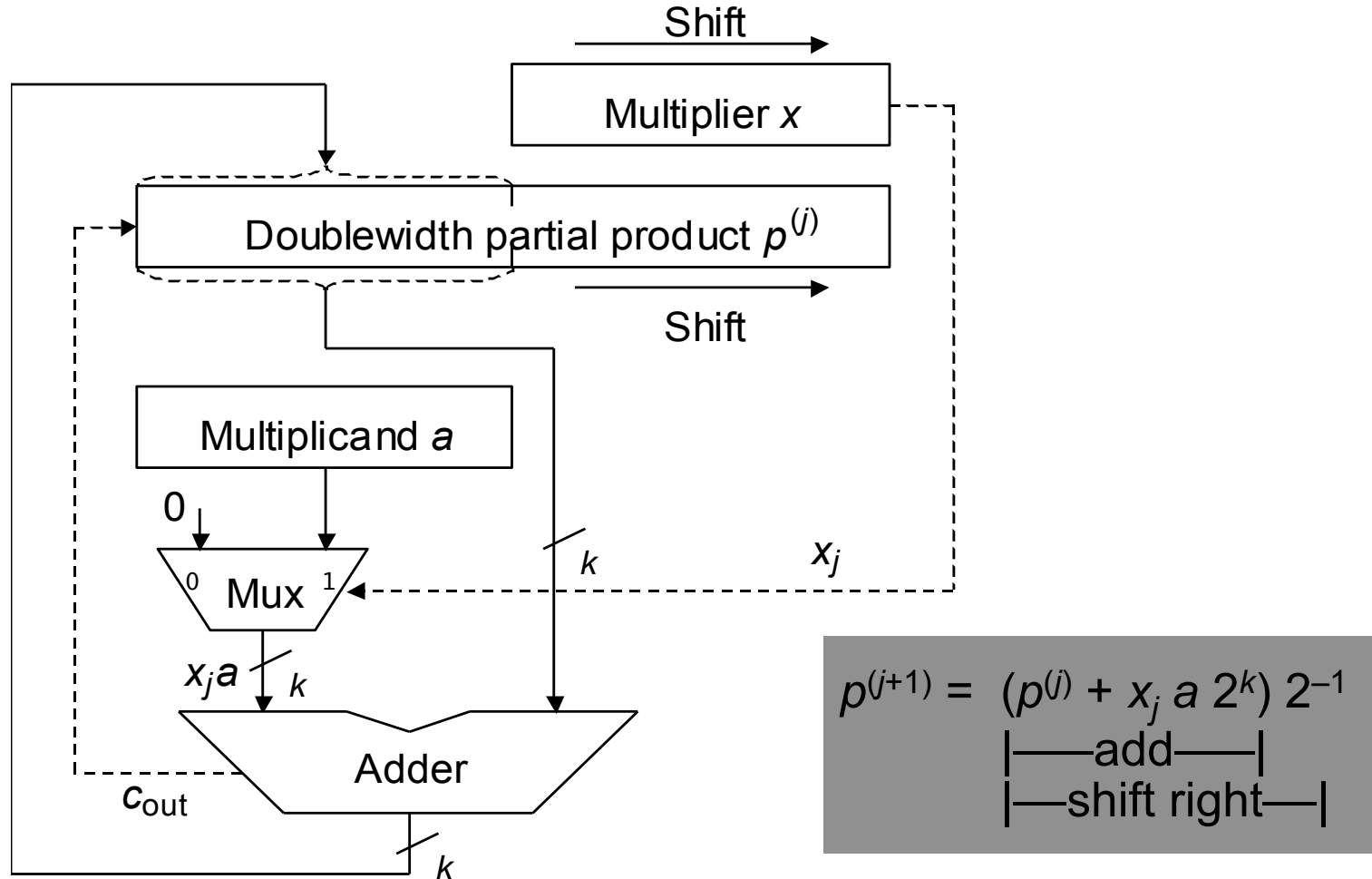


Fig. 9.4 Hardware realization of the sequential multiplication algorithm with additions and right shifts.

EXAMPLE OF HARDWARE MULTIPLICATION

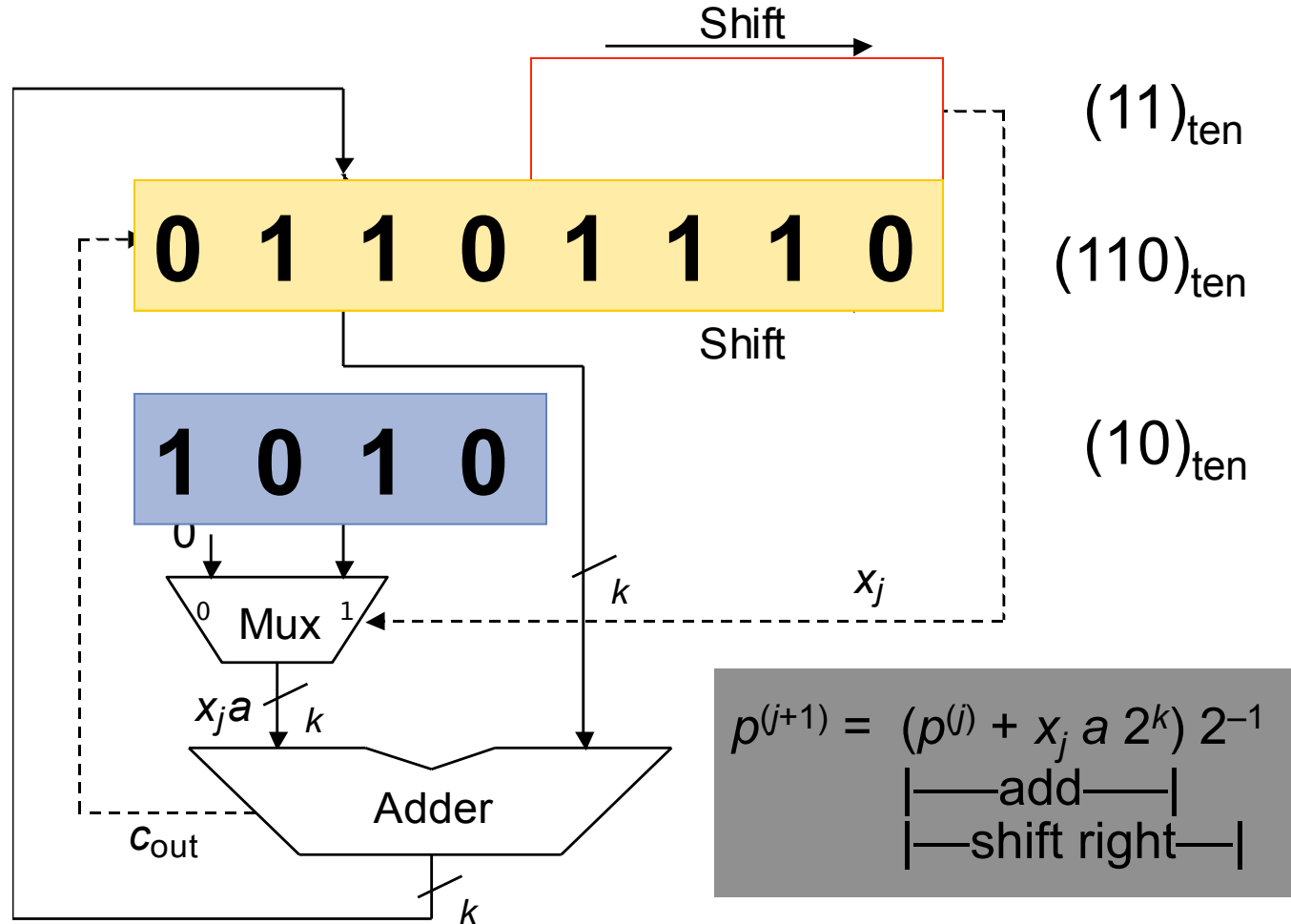


Fig. 9.4a Hardware realization of the sequential multiplication algorithm with additions and right shifts.

SEQUENTIAL MULTIPLICATION WITH LEFT SHIFTS

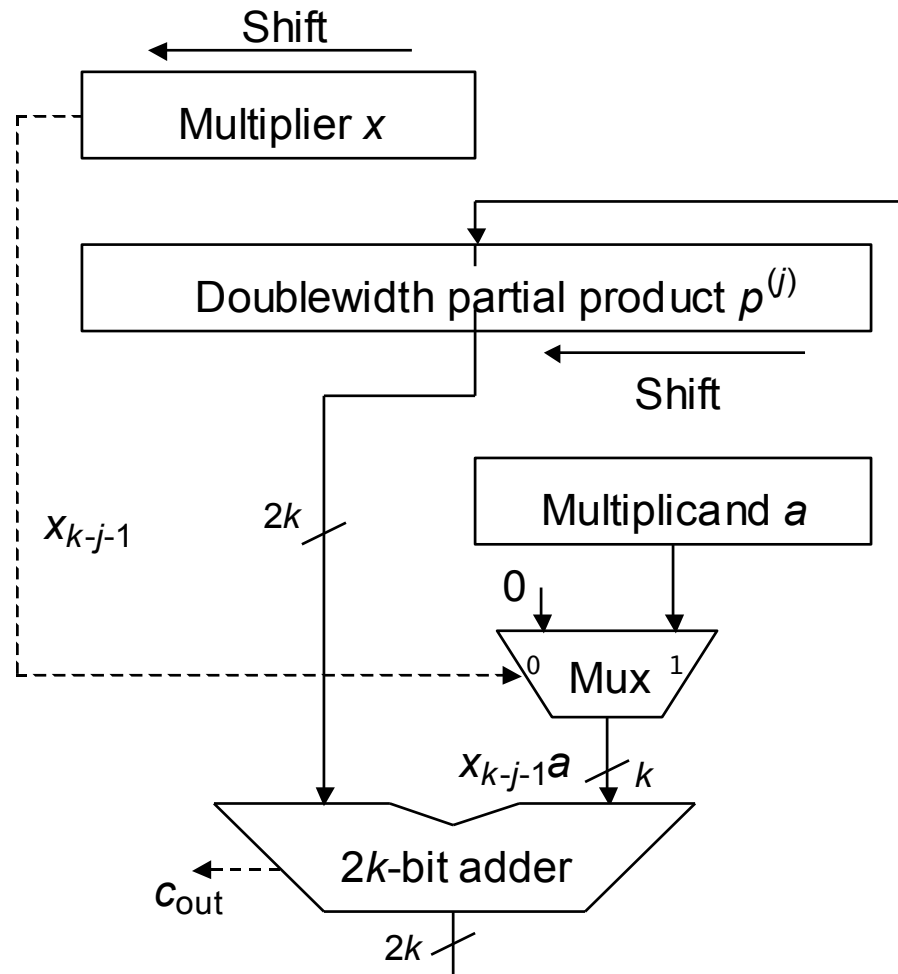


Fig. 9.4b Hardware realization of the sequential multiplication algorithm with left shifts and additions.

9.4 MULTIPLICATION OF SIGNED NUMBERS

Fig. 9.6 Sequential multiplication of 2' s-complement numbers with right shifts (positive multiplier).

Negative multiplicand,
positive multiplier:

No change, other than
looking out for proper
sign extension

Check:

$$-10 \times 11 = -110 = -512 + 256 + 128 + 16 + 2$$

=====									
<i>a</i>		1	0	1	1	0			
<i>x</i>		0	1	0	1	1			
=====									
<i>p</i> ⁽⁰⁾		0	0	0	0	0			
+ <i>x</i> ₀ <i>a</i>		1	0	1	1	0			
<hr/>									
2 <i>p</i> ⁽¹⁾	1	1	0	1	1	0			
<i>p</i> ⁽¹⁾		1	1	0	1	1	0		
+ <i>x</i> ₁ <i>a</i>		1	0	1	1	0			
<hr/>									
2 <i>p</i> ⁽²⁾	1	1	0	0	0	1	0		
<i>p</i> ⁽²⁾		1	1	0	0	0	1	0	
+ <i>x</i> ₂ <i>a</i>		0	0	0	0	0			
<hr/>									
2 <i>p</i> ⁽³⁾	1	1	1	0	0	0	1	0	
<i>p</i> ⁽³⁾		1	1	1	0	0	0	1	0
+ <i>x</i> ₃ <i>a</i>		1	0	1	1	0			
<hr/>									
2 <i>p</i> ⁽⁴⁾	1	1	0	0	1	0	0	1	0
<i>p</i> ⁽⁴⁾		1	1	0	0	1	0	0	1
+ <i>x</i> ₄ <i>a</i>		0	0	0	0	0			
<hr/>									
2 <i>p</i> ⁽⁵⁾	1	1	1	0	0	1	0	0	1
<i>p</i> ⁽⁵⁾		1	1	1	0	0	1	0	0
=====									

THE CASE OF A NEGATIVE MULTIPLIER

Fig. 9.7 Sequential multiplication of 2' s-complement numbers with right shifts (negative multiplier).

Negative multiplicand,
negative multiplier:

In last step (the sign bit),
subtract rather than add

Check:

$$-10 \times -11 = 110 = 64 + 32 + 8 + 4 + 2$$

=====									
a		1	0	1	1	0			
x		1	0	1	0	1			
=====									
$p^{(0)}$		0	0	0	0	0			
$+x_0a$		1	0	1	1	0			
<hr/>									
$2p^{(1)}$	1	1	0	1	1	0			
$p^{(1)}$		1	1	0	1	1	0		
$+x_1a$		0	0	0	0	0			
<hr/>									
$2p^{(2)}$	1	1	1	0	1	1	0		
$p^{(2)}$		1	1	1	0	1	1	0	
$+x_2a$		1	0	1	1	0			
<hr/>									
$2p^{(3)}$	1	1	0	0	1	1	1	0	
$p^{(3)}$		1	1	0	0	1	1	1	0
$+x_3a$		0	0	0	0	0			
<hr/>									
$2p^{(4)}$	1	1	1	0	0	1	1	1	0
$p^{(4)}$		1	1	1	0	0	1	1	1
$+(-x_4a)$		0	1	0	1	0			
<hr/>									
$2p^{(5)}$	0	0	0	1	1	0	1	1	1
$p^{(5)}$		0	0	0	1	1	0	1	1
=====									

SIGNED 2' S-COMPLEMENT HARDWARE MULTIPLIER

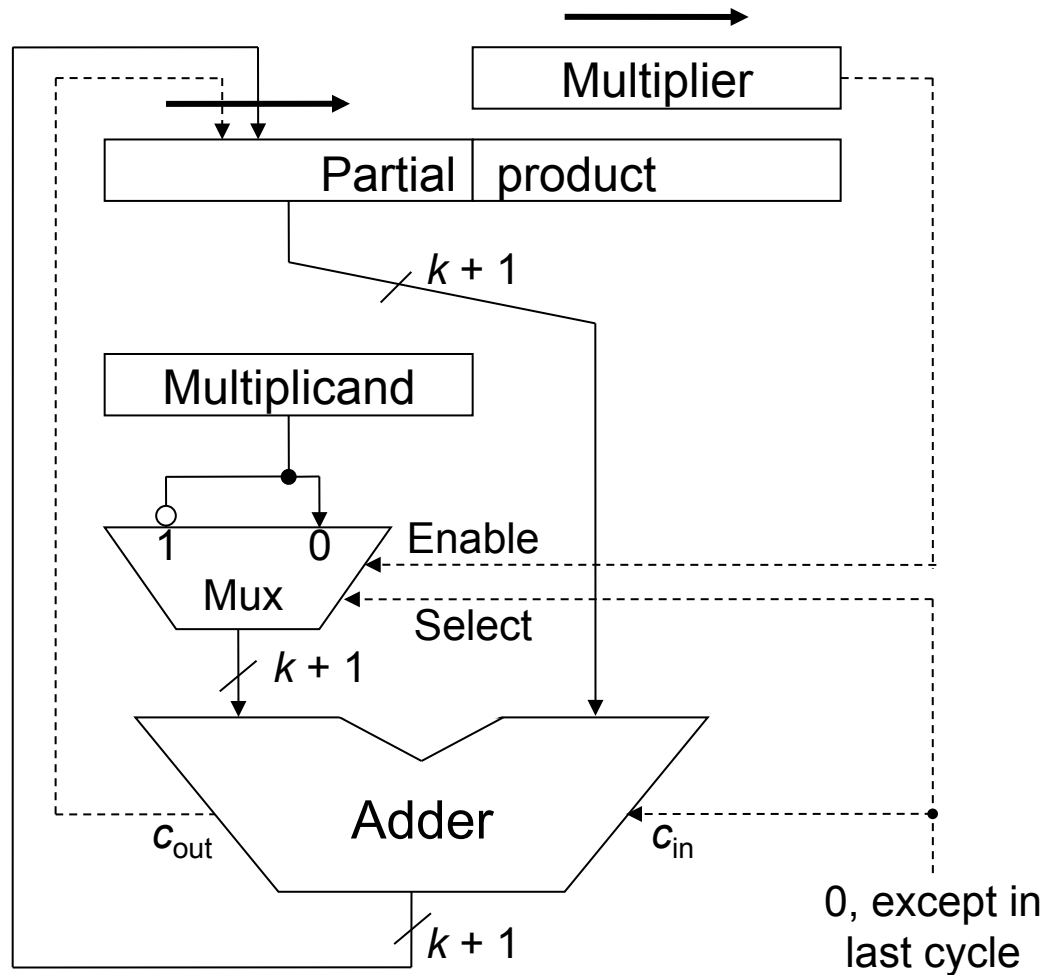


Fig. 9.8 The 2' s-complement sequential hardware multiplier.

BOOTH' S RECODING

Table 9.1 Radix-2 Booth' s recoding

x_i	x_{i-1}	y_i	Explanation
0	0	0	No string of 1s in sight
0	1	1	End of string of 1s in x
1	0	-1	Beginning of string of 1s in x
1	1	0	Continuation of string of 1s in x

Example

1	0	0	1	1	1	0	1	1	0	1	0	1	1	1	0	Operand x	
(1)	-1	0	1	0	0	-1	1	0	-1	1	-1	1	0	0	-1	0	Recoded version y

Justification

$$2^j + 2^{j-1} + \dots + 2^{i+1} + 2^i = 2^{j+1} - 2^i$$

EXAMPLE MULTIPLICATION WITH BOOTH'S RECODING

Fig. 9.9 Sequential multiplication of 2's-complement numbers with right shifts by means of Booth's recoding.

x_i	x_{i-1}	y_i
0	0	0
0	1	1
1	0	-1
1	1	0

Check:

$$-10 \times -11 = 110 = 64 + 32 + 8 + 4 + 2$$

a	1	0	1	1	0						
x	1	0	1	0	1	Multiplier					
y	-1	1	-1	1	-1	Booth-recoded					
=====											
$p^{(0)}$	0	0	0	0	0						
$+y_0a$	0	1	0	1	0						

$2p^{(1)}$	0	0	1	0	1	0					
$p^{(1)}$	0	0	1	0	1	0					
$+y_1a$	1	0	1	1	0						

$2p^{(2)}$	1	1	1	0	1	1	0				
$p^{(2)}$	1	1	1	0	1	1	0				
$+y_2a$	0	1	0	1	0						

$2p^{(3)}$	0	0	0	1	1	1	1	0			
$p^{(3)}$	0	0	0	1	1	1	1	0			
$+y_3a$	1	0	1	1	0						

$2p^{(4)}$	1	1	1	0	0	1	1	1	0		
$p^{(4)}$	1	1	1	0	0	1	1	1	0		
y_4a	0	1	0	1	0						

$2p^{(5)}$	0	0	0	1	1	0	1	1	1	0	
$p^{(5)}$	0	0	0	1	1	0	0	1	1	1	0
=====											

PROBLEMAS

Problema 9.1. Faça a multiplicação 42×43 usando:

- a) Algoritmo *Shift-Left*.
- b) Algoritmo *Shift-Right*.

Problema 9.2. Faça a multiplicação -5×-3 usando:


- a) Algoritmo *Shift-Right* com recodificação de *Booth*.

9.5 MULTIPLICATION BY CONSTANTS

Multiplication Using Binary Expansion

Example: Multiply R1 by the constant 113 = $(1\ 1\ 1\ 0\ 0\ 0\ 1)_{\text{two}}$

R2	←	R1 shift-left 1
R3	←	R2 + R1
R6	←	R3 shift-left 1
R7	←	R6 + R1
R112	←	R7 shift-left 4
R113	←	R112 + R1

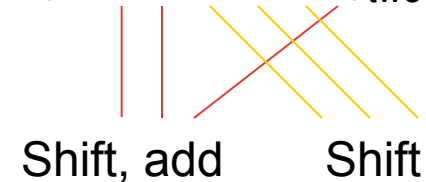

R_i : Register that contains i times (R1)

This notation is for clarity; only one register other than R1 is needed

Shorter sequence using shift-and-add instructions

R3	←	R1 shift-left 1 + R1
R7	←	R3 shift-left 1 + R1
R113	←	R7 shift-left 4 + R1

MULTIPLICATION VIA RECODING


Example: Multiply R1 by $113 = (1\ 1\ 1\ 0\ 0\ 0\ 1)_{\text{two}} = (1\ 0\ 0\ -1\ 0\ 0\ 0\ 1)_{\text{two}}$

R8 \leftarrow R1 shift-left 3

R7 \leftarrow R8 - R1

R112 \leftarrow R7 shift-left 4

R113 \leftarrow R112 + R1

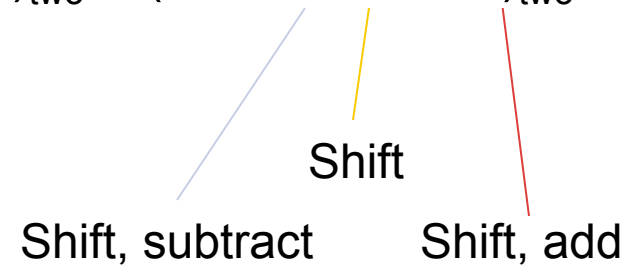

Shorter sequence using shift-and-add/subtract instructions

R7 \leftarrow R1 shift-left 3 - R1

R113 \leftarrow R7 shift-left 4 + R1

6 shift or add (3 shift-and-add) instructions needed without recoding

MULTIPLICATION VIA FACTORIZATION

Example: Multiply R1 by $119 = 7 \times 17 = (8 - 1) \times (16 + 1)$

```
R8      ←      R1 shift-left 3
R7      ←      R8 - R1
R112    ←      R7 shift-left 4
R119    ←      R112 + R7
```

Shorter sequence using shift-and-add/subtract instructions

```
R7      ←      R1 shift-left 3 - R1
R119    ←      R7 shift-left 4 + R7
```

Requires a scratch register
for holding the 7 multiple

MULTIPLICATION BY MULTIPLE CONSTANTS

Example: Multiplying a number by 45, 49, and 65

R9	←	R1 shift-left 3 + R1	} Separate solutions: 5 shift-add/subtract operations
R45	←	R9 shift-left 2 + R9	
R7	←	R1 shift-left 3 - R1	
R49	←	R7 shift-left 3 - R7	
R65	←	R1 shift-left 6 + R1	

A combined solution for all three constants

R65	←	R1 shift-left 6 + R1
R49	←	R65 - R1 left-shift 4
R45	←	R49 - R1 left-shift 2

A programmable block can perform any of the three multiplications

PROBLEMAS

Problema 9.3. Faça as seguintes multiplicações por constante a nível de transferência de registradores (RTL design):

- a) $43 \times A$
- b) $129 \times A$
- c) $63 \times A$
- d) $945 \times A$
- e) $4,5 \times A$

Problema 9.4. Na multiplicação $978943 \times A$


- a) Faça a compressão direta da informação.
- b) Use dois níveis de CSAs com os múltiplos de 7 no reconhecimento de padrão.

Problema 9.5. Na multiplicação $93177183807 \times A$:

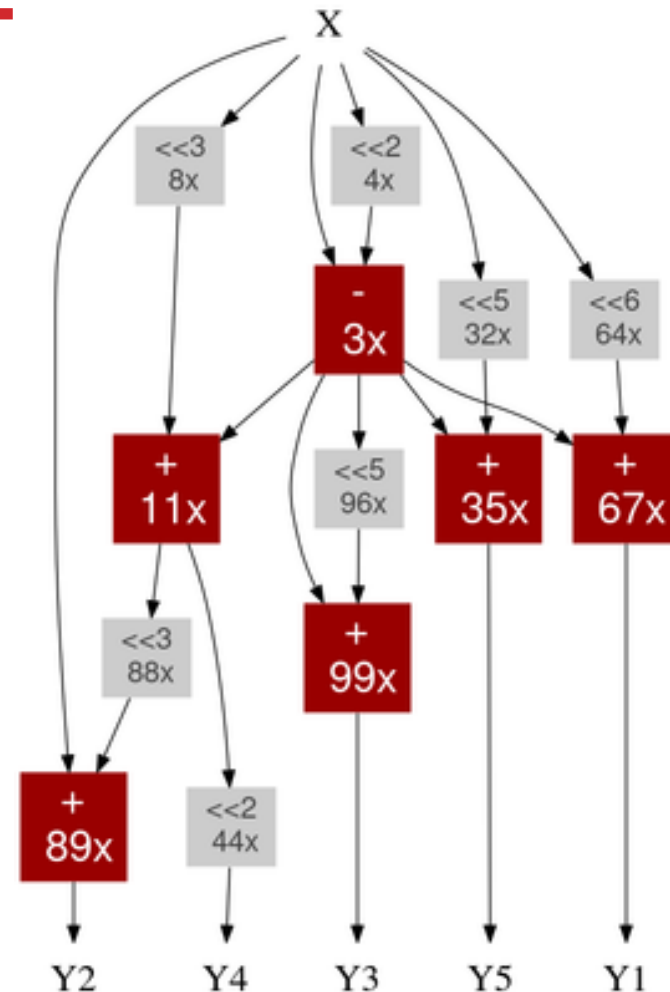- a) Faça a compressão direta da informação.
- b) Use dois níveis de CSAs com os múltiplos de 21 no reconhecimento de padrão (pode usar os múltiplos ímpares até 21). Obtenha o custo e caminho crítico considerando A_{FA} e T_{FA} como a área e atraso por *Full-Adder*.

MULTIPLICATION BY MULTIPLE CONSTANTS: HCUB SOFTWARE TOOL

Fazer a multiplicação pelo conjunto
{67,89,99,44,35}



<http://spiral.ece.cmu.edu/mcm/gen.html>

PROBLEMAS


Problema 9.6. A partir dos ferramenta que obtém o grafo associado à multiplicação de múltiplas constantes obtenha:

- a) O grafo para a obtenção dos números primos 3, 5, 11, 13, 37, 41 e 43 (para a geração do grafo use *Fractional bits*: 0, *Algortihm*: Hcub e *Depth Limit*: Minimum possible)
- b) O que poderia ser feito para melhorar a eficiência tendo em consideração que o substrator é uma unidade maior e com maior atraso que um somador?
- c) Use agora *Algortihm*: BHM na ferramenta e reduza o número de níveis.

MULTIPLICATION BY MULTIPLE CONSTANTS: ANOTHER EXAMPLE

Desenhe um circuito aritmético com uma entrada de seleção de dois bits, $S = s_1s_0$, que realize as operações aritméticas mostradas na tabela usando unicamente um somador de 8 bits com carry in e carry out e multiplexadores 4:1. Suponha A , B , C e D entradas de 4-bits sendo a entrada A uma entrada sempre par.



S	F
00	$F = 3A + 560B + 256C + 4096D + 16389$
01	$F = 0,5A + 25B + 4224C + 4352D + 2049$
10	$F = 8499B + 6144$
11	$F = \frac{(9393A + 4096B + 256C + 164)}{2}$

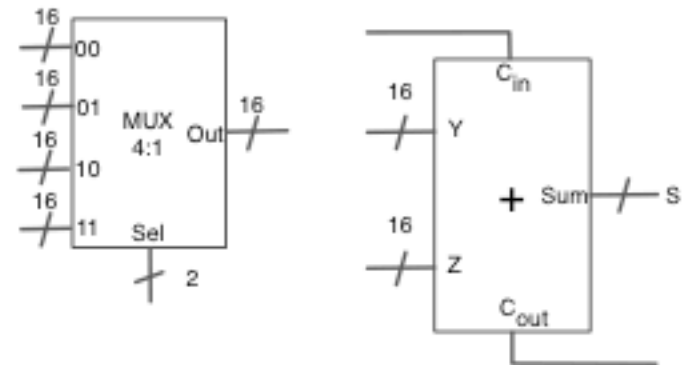

PROBLEMAS

Problema 9.7. Desenhe um circuito aritmético com uma entrada de seleção de dois bits, $S=s1s0$, que realize as operações aritméticas mostradas na tabela usando unicamente um somador de 8 bits com *carry in* e *carry out* e multiplexadores 4:1. Suponha A , B , C e D entradas de 4-bits sendo a entrada A uma entrada sempre par.

S	F
00	$F = 3A + 560B + 256C + 4096D + 16389$
01	$F = 0,5A + 25B + 4224C + 4352D + 2049$
10	$F = 8499B + 6144$
11	$F = \frac{(9393A + 4096B + 256C + 164)}{2}$

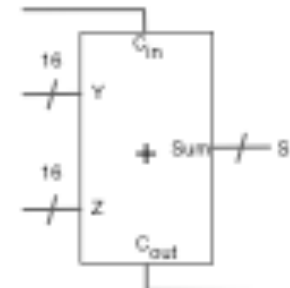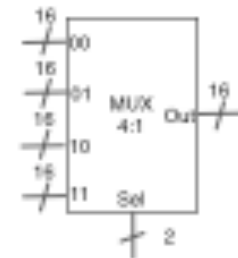

MULTIPLICATION BY MULTIPLE CONSTANTS: EXAMPLE

Solução:


As entradas são:

$$A = a_3 a_2 a_1 a_0 = a_3 a_2 a_1 0.$$

$$B = b_3 b_2 b_1 b_0.$$

$$C = c_3 c_2 c_1 c_0.$$

$$D = d_3 d_2 d_1 d_0.$$

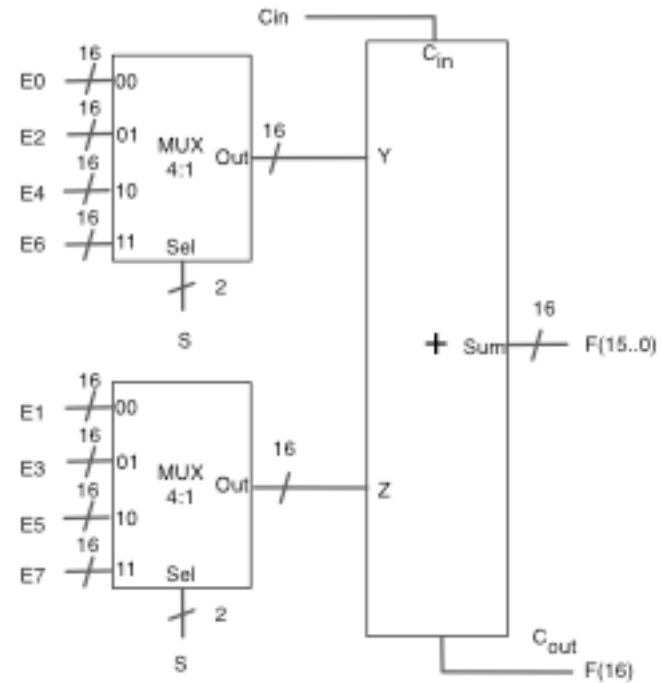

MULTIPLICATION BY MULTIPLE CONSTANTS: EXAMPLE

Temos de inserir nas entradas E_i a informação das operações de multiplicação por constante. A tabela seguinte contém a informação a ser inserida.

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	cin
E0	d3	d2	d1	d0	c3	c2	c1	c0	b3	b2	b1	b0	a3	a2	a1	1	1
E1	0	1	0	b3	b2	b1	b0	b3	b2	b1	b0	a3	a2	a1	1	1	
E2	c3	c2	c1	c0	1	c3	c2	c1	c0	b3	b2	b1	b0	a3	a2	a1	1
E3	d3	d2	d1	d0	d3	d2	d1	d0	b3	b2	b1	b0	b3	b2	b1	b0	
E4	b3	b2	b1	b0	b3	b2	b1	b0	b3	b2	b1	b0	b3	b2	b1	b0	1
E5	b3	b2	b1	b0	1	1	0	b3	b2	b1	b0	b3	b2	b1	b0	1	
E6	a3	a2	a1	a3	a2	a1	a3	a2	a1	a3	a2	a1	a3	a2	a1	1	1
E7	0	b3	b2	b1	b0	c3	c2	c1	c0	1	0	1	0	a3	a2	a1	

Para F quando $S=0$ (soma de E0 com E1).

$$F=(2^1+2^0)A+(2^9+2^5+2^4)B+(2^8)C+(2^{12})D+(2^{14}+2^2+2^0).$$

Para F quando $S=1$ (soma de E2 com E3).

$$F=(2^{-1})A+(2^4+2^3+2^0)B+(2^{12}+2^7)C+(2^{12}+2^8)D+(2^{11}+2^0).$$

Para F quando $S=2$ (soma de E4 com E5).

$$F=(2^{13}+2^8+2^5+2^4+2^1+2^0)B+(2^{11}+2^{10}+2^1).$$

Para F quando $S=3$ (soma de E6 com E7) numerador da divisão.

$$F=(2^{13}+2^{10}+2^7+2^4+2^1+2^0)A+(2^{12})B+(2^8)C+(2^7+2^5+2^1).$$