

6 CARRY-LOOKAHEAD ADDERS AND VARIATIONS IN FAST ADDERS

Chapter Goals

Understand the carry-lookahead method and its many variations used in the design of fast adders

Study alternatives to the carry-lookahead method for designing fast adders

Chapter Highlights

Single- and multilevel carry lookahead

Various designs for log-time adders

Relating the carry determination problem to parallel prefix computation

Implementing fast adders in VLSI

CARRY-LOOKAHEAD ADDERS AND VARIATIONS IN FAST ADDERS: TOPICS

Topics in This Chapter

6.1 Unrolling the Carry Recurrence

6.2 Carry-Lookahead Adder Design

6.4 Carry Determination as Prefix Computation

6.5 Alternative Parallel Prefix Networks

7.3 Carry-Select Adders

7.4 Analysis of Carry Propagation

7.6 Modular Two-Operand Adders

6.1 UNROLLING THE CARRY RECURRENCE


Recall the *generate*, *propagate*, *annihilate* (*absorb*), and *transfer* signals:

<u>Signal</u>	<u>Binary</u>
g_i	$x_i y_i$
p_i	$x_i \oplus y_i$
a_i	$x_i' y_i' = (x_i \vee y_i)'$
t_i	$x_i \vee y_i$
s_i	$x_i \oplus y_i \oplus c_i$

The carry recurrence can be unrolled to obtain each carry signal directly from inputs, rather than through propagation

$$\begin{aligned}c_i &= g_{i-1} \vee c_{i-1} p_{i-1} \\&= g_{i-1} \vee (g_{i-2} \vee c_{i-2} p_{i-2}) p_{i-1} \\&= g_{i-1} \vee g_{i-2} p_{i-1} \vee c_{i-2} p_{i-2} p_{i-1} \\&= g_{i-1} \vee g_{i-2} p_{i-1} \vee g_{i-3} p_{i-2} p_{i-1} \vee c_{i-3} p_{i-3} p_{i-2} p_{i-1} \\&= g_{i-1} \vee g_{i-2} p_{i-1} \vee g_{i-3} p_{i-2} p_{i-1} \vee g_{i-4} p_{i-3} p_{i-2} p_{i-1} \vee c_{i-4} p_{i-4} p_{i-3} p_{i-2} p_{i-1} \\&= \dots\end{aligned}$$

FULL CARRY LOOKAHEAD

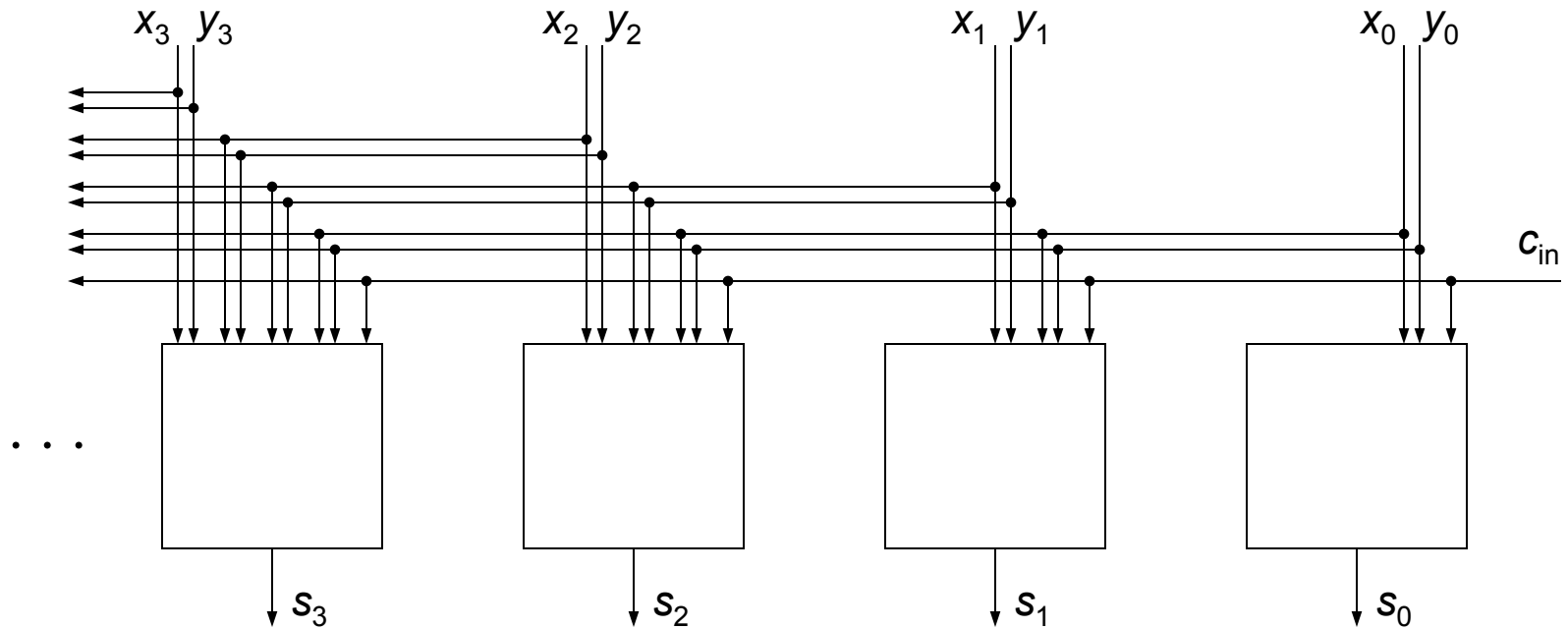

Theoretically, it is possible to derive each sum digit directly from the inputs that affect it

Carry-lookahead adder design is simply a way of reducing the complexity of this ideal, but impractical, arrangement by hardware sharing among the various lookahead circuits

FOUR-BIT CARRY-LOOKAHEAD ADDER

Complexity
reduced by
deriving the
carry-out
indirectly

Full carry lookahead is quite practical
for a 4-bit adder

$$c_1 = g_0 \vee c_0 p_0$$

$$c_2 = g_1 \vee g_0 p_1 \vee c_0 p_0 p_1$$

$$c_3 = g_2 \vee g_1 p_2 \vee g_0 p_1 p_2 \vee c_0 p_0 p_1 p_2$$

$$c_4 = g_3 \vee g_2 p_3 \vee g_1 p_2 p_3 \vee g_0 p_1 p_2 p_3 \\ \vee c_0 p_0 p_1 p_2 p_3$$

 


Fig. 6.1 Four-bit carry network with full lookahead.

CARRY LOOKAHEAD BEYOND 4 BITS

Consider a 32-bit adder

$$c_1 = g_0 \vee c_0 p_0$$

$$c_2 = g_1 \vee g_0 p_1 \vee c_0 p_0 p_1$$

$$c_3 = g_2 \vee g_1 p_2 \vee g_0 p_1 p_2 \vee c_0 p_0 p_1 p_2$$

⋮
⋮
⋮

$$c_{31} = g_{30} \vee g_{29} p_{30} \vee g_{28} p_{29} p_{30} \vee g_{27} p_{28} p_{29} p_{30} \vee \dots \vee c_0 p_0 p_1 p_2 p_3 \dots p_{29} p_{30}$$

No circuit sharing:
Repeated computations

32-input AND

32-input OR

High fan-ins necessitate
tree-structured circuits

ONE SOLUTION TO THE FAN-IN PROBLEM

Multilevel lookahead

Example: 16-bit addition

Radix-16 (four digits)

Two-level carry lookahead (four 4-bit blocks)

Either way, the carries c_4 , c_8 , and c_{12} are determined first

c_{16}	c_{15}	c_{14}	c_{13}	c_{12}	c_{11}	c_{10}	c_9	c_8	c_7	c_6	c_5	c_4	c_3	c_2	c_1	c_0
c_{out}				?				?				?				c_{in}

6.2 CARRY-LOOKAHEAD ADDER DESIGN

Block *generate* and *propagate* signals

$$g_{[i,i+3]} = g_{i+3} \vee g_{i+2}p_{i+3} \vee g_{i+1}p_{i+2}p_{i+3} \vee g_i p_{i+1}p_{i+2}p_{i+3}$$

$$p_{[i,i+3]} = p_i p_{i+1} p_{i+2} p_{i+3}$$


 
 



Fig. 6.2b Schematic diagram of a 4-bit lookahead carry generator.

A BUILDING BLOCK FOR CARRY-LOOKAHEAD ADDITION

Fig. 6.2a A 4-bit
lookahead
carry generator

 

A TWO-LEVEL CARRY-LOOKAHEAD ADDER

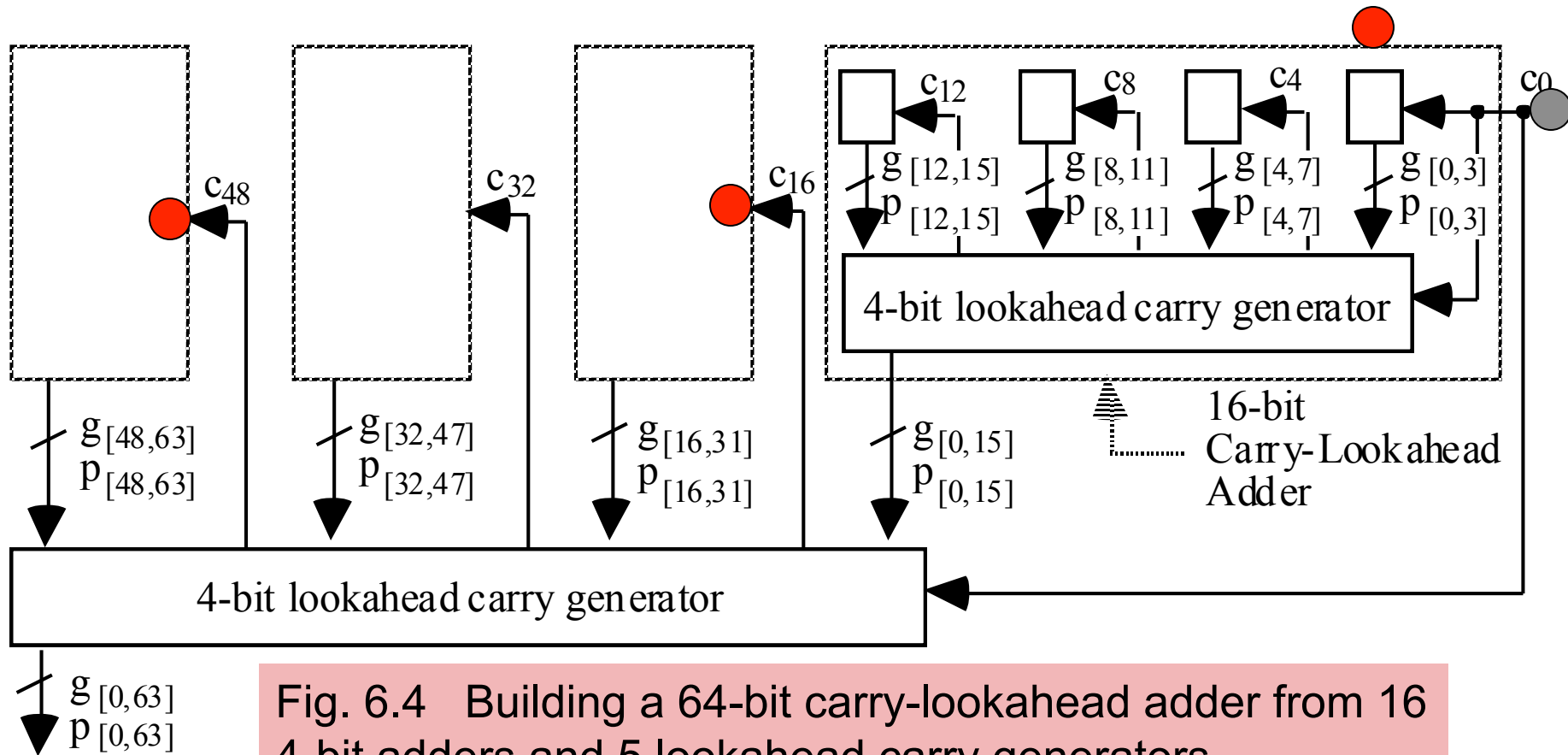

Carry-out:
$$c_{\text{out}} = g_{[0,k-1]} \vee c_0 p_{[0,k-1]} = x_{k-1} y_{k-1} \vee s_{k-1}' (x_{k-1} \vee y_{k-1})$$

6.4 CARRY DETERMINATION AS PREFIX COMPUTATION

 


Fig. 6.5 Combining of g and p signals of two (contiguous or overlapping) blocks B' and B'' of arbitrary widths into the g and p signals for block B.

FORMULATING THE PREFIX COMPUTATION PROBLEM

The problem of carry determination can be formulated as:

Given $(g_0, p_0) \quad (g_1, p_1) \quad . \quad . \quad . \quad (g_{k-2}, p_{k-2}) \quad (g_{k-1}, p_{k-1})$
 Find $(g_{[0,0]}, p_{[0,0]}) \quad (g_{[0,1]}, p_{[0,1]}) \quad . \quad . \quad . \quad (g_{[0,k-2]}, p_{[0,k-2]}) \quad (g_{[0,k-1]}, p_{[0,k-1]})$
 $\downarrow \quad \quad \quad \downarrow \quad \quad \quad . \quad . \quad . \quad \downarrow \quad \quad \quad \downarrow$
 $c_1 \quad \quad \quad c_2 \quad \quad \quad . \quad . \quad . \quad c_{k-1} \quad \quad \quad c_k$

Carry-in can be viewed as an extra (-1) position: $(g_{-1}, p_{-1}) = (c_{in}, 0)$

The desired pairs are found by evaluating all prefixes of

$(g_0, p_0) \phi (g_1, p_1) \phi . \quad . \quad . \quad \phi (g_{k-2}, p_{k-2}) \phi (g_{k-1}, p_{k-1})$
 $\xrightarrow{\hspace{1.5cm}}$
 $\xrightarrow{\hspace{4.5cm}}$

The carry operator ϕ is associative, but not commutative

$$[(g_1, p_1) \phi (g_2, p_2)] \phi (g_3, p_3) = (g_1, p_1) \phi [(g_2, p_2) \phi (g_3, p_3)]$$

Prefix sums analogy:

Given $x_0 \quad x_1 \quad x_2 \quad . \quad . \quad . \quad x_{k-1}$
 Find $x_0 \quad x_0+x_1 \quad x_0+x_1+x_2 \quad . \quad . \quad . \quad x_0+x_1+\dots+x_{k-1}$

6.5 ALTERNATIVE PARALLEL PREFIX NETWORKS


 


Fig. 6.7 Ladner-Fischer parallel prefix sums network built of two $k/2$ -input networks and $k/2$ adders.

Delay recurrence $D(k) = D(k/2) + 1 = \log_2 k$

 Cost recurrence $C(k) = 2C(k/2) + k/2 = (k/2) \log_2 k$



LADNER-FISHER

DELAY=4

COST=32

COST x DELAY=128

THE BRENT-KUNG RECURSIVE CONSTRUCTION

 


Fig. 6.8 Parallel prefix sums network built of one $k/2$ -input network and $k - 1$ adders.


Delay recurrence

$$D(k) = D(k/2) + 2 = 2 \log_2 k - 1 \quad (-2 \text{ really})$$


Cost recurrence

$$C(k) = C(k/2) + k - 1 = 2k - 2 - \log_2 k$$

BRENT-KUNG CARRY NETWORK (8-BIT ADDER)

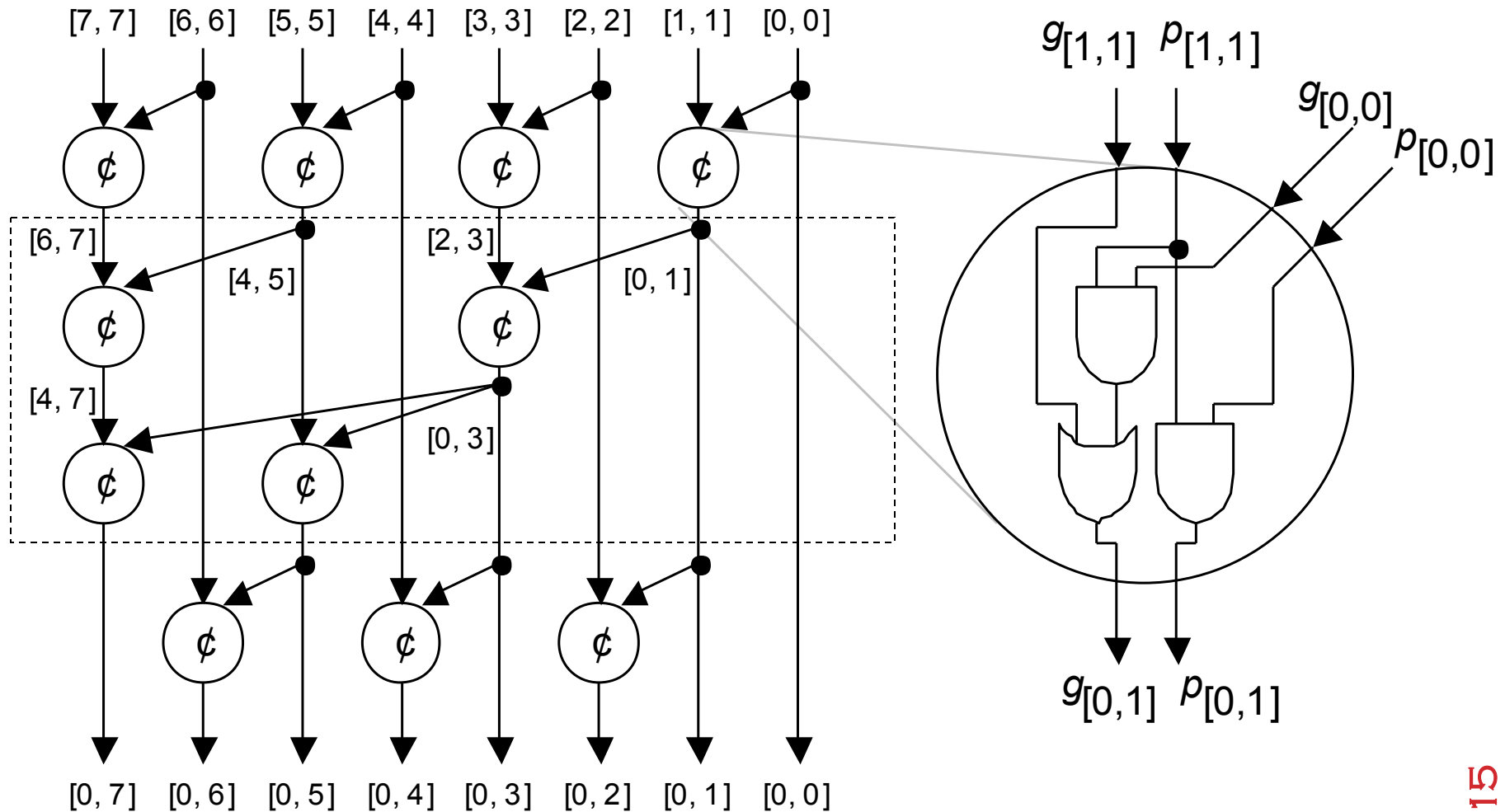

BRENT-KUNG CARRY NETWORK (16-BIT ADDER)

 


KOGGE-STONE CARRY NETWORK (16-BIT ADDER)

Cost formula
 $C(k) = (k - 1)$
+ $(k - 2)$
+ $(k - 4) + \dots$
+ $(k - k/2)$
 $= k \log_2 k - k + 1$


$\log_2 k$ levels
(minimum possible)

Fig. 6.10
Kogge-Stone
parallel prefix
graph for
16 inputs.

 

HYBRID B-K/K-S (HAN CARLSON) CARRY NETWORK (16-BIT)

Brent-Kung:
6 levels
26 cells

 

Kogge-Stone:
4 levels
49 cells


 


Fig. 6.11
A Hybrid
Brent-Kung/
Kogge-Stone
parallel prefix
graph for
16 inputs.

 

Hybrid:
5 levels
32 cells

SPEED-COST TRADEOFFS IN CARRY NETWORKS

Method	Delay	Cost
Ladner-Fischer	$\log_2 k$	$(k/2) \log_2 k$
Kogge-Stone	$\log_2 k$	$k \log_2 k - k + 1$
Brent-Kung	$2 \log_2 k - 2$	$2k - 2 - \log_2 k$
Han Carlson	$\log_2 k + 1$	$(k/2) \log_2 k$

k= 16-bits

Method	Delay	Cost
Ladner-Fischer	4	32
Kogge-Stone	4	49
Brent-Kung	6	26
Han Carlson	5	32

PROBLEMAS

Problema 6.1 Obtenha os gráficos para valores pares $n \in [4, 32]$ dos somadores Ladner-Fisher (LF), Brent-Kung (BK), Kogge-Stone (KS), e Han-Carlson (HC) para:

- a) Área.
- b) Atraso.
- c) Produto área atraso (AT)
- d) Produto área atraso quadrado (AT^2).
- e) Fan-out.

Indique qual é a melhor opção para as diferentes figuras de mérito apresentadas acima.

7.3 CARRY-SELECT ADDERS

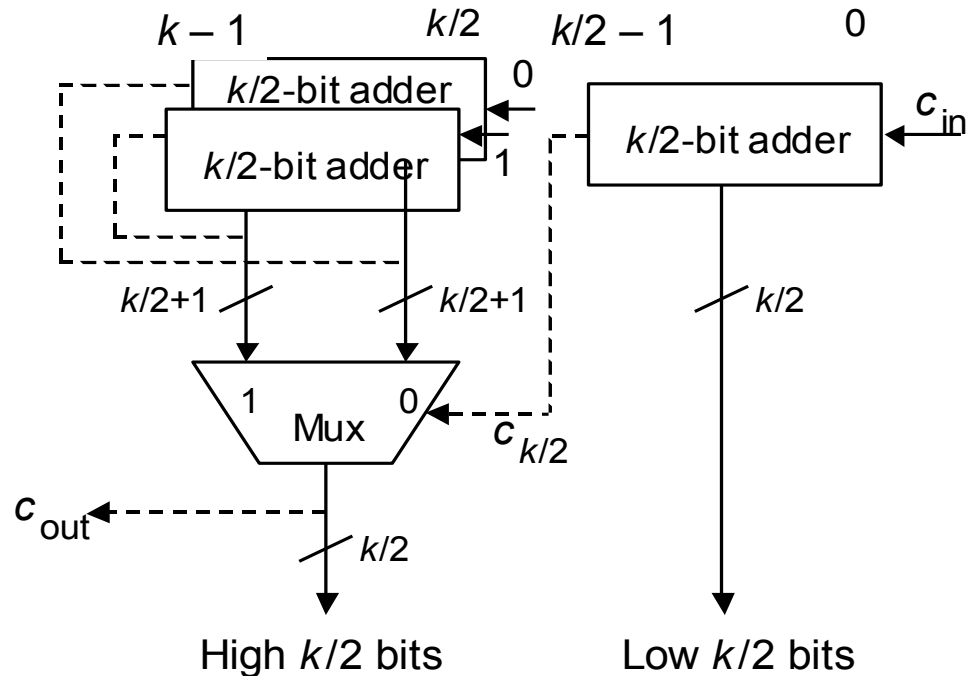


Fig. 7.9 Carry-select adder for k -bit numbers built from three $k/2$ -bit adders.

$$C_{\text{select-add}}(k) = 3C_{\text{add}}(k/2) + k/2 + 1$$

$$T_{\text{select-add}}(k) = T_{\text{add}}(k/2) + 1$$

MULTILEVEL CARRY-SELECT ADDERS

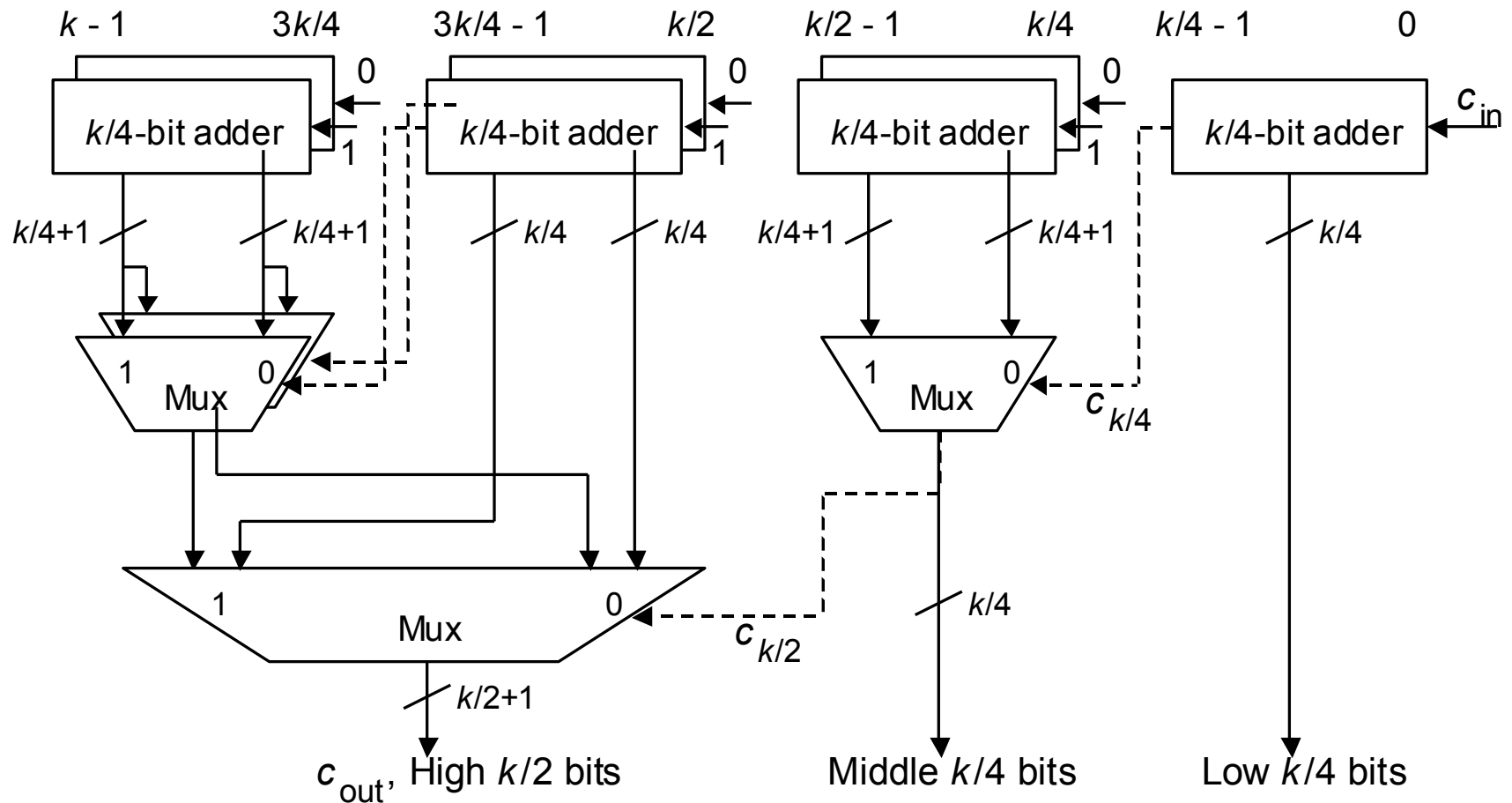


Fig. 7.10 Two-level carry-select adder built of $k/4$ -bit adders.

PROBLEMAS

Problema 6.2 Faça uma otimização para um *Carry-Select-Adder* de 64-bits dividido em 4 somas e assumindo que a área e o atraso do somador está expressado como $n \times A_{adder}$, $n \times T_{adder}$, respectivamente, sendo n o número de bits. Considere a área e atraso do multiplexador 2:1 como uma unidade $(2/3) \times A_{adder}$, $(2/3) \times T_{adder}$.

7.4 ANALYSIS OF CARRY PROPAGATION

 


Fig. 7.11 Example addition and its carry propagation chains.

Given binary numbers with random bits, for each position i we have

Probability of carry generation = $\frac{1}{4}$ (both 1s)

Probability of carry annihilation = $\frac{1}{4}$ (both 0s)

Probability of carry propagation = $\frac{1}{2}$ (different)

PROBLEMAS

Problema 6.3. Uma entrada fixa $A = 31727_{10}$ deve ser somada com entradas variáveis B e C, todas de 16-bits. Ditas entradas variáveis só podem ter os seguintes valores:

- $B = \{2638_{10}, 31439_{10}, 14923_{10}\}.$
- $C = \{3041_{10}, 15343_{10}, 3192_{10}\}.$

Qual das somas pode ser implementada com um atraso menor?

Problema 6.4. Dois vetores de 12 bits A e B precisam de ser somados, onde A é sempre múltiplo $100_{(10)}$ e B múltiplo de $48_{(10)}$. Considerando os tempos de atraso do problema 6.2, obtenha a soma dos vectores com um atraso máximo de $5 \times T_{adder}$

7.6 MODULAR TWO-OPERAND ADDERS

$\text{mod-}2^k$: Ignore carry out of position $k - 1$

$\text{mod-}(2^k - 1)$: Use End-Around Carry (EAC)

$\text{mod-}(2^k + 1)$: Use Inverted End-Around Carry (IEAC)

Number	Std. binary
0	0 0 . . . 0 0 0
1	0 0 . . . 0 0 1
2	0 0 . . . 0 1 0
.	.
.	.
.	.
$2^k - 1$	0 1 . . . 1 1 1
2^k	1 0 . . . 0 0 0

GENERAL MODULAR ADDERS

$$(x + y) \bmod m$$

if $x + y \geq m$
then $x + y - m$
else $x + y$

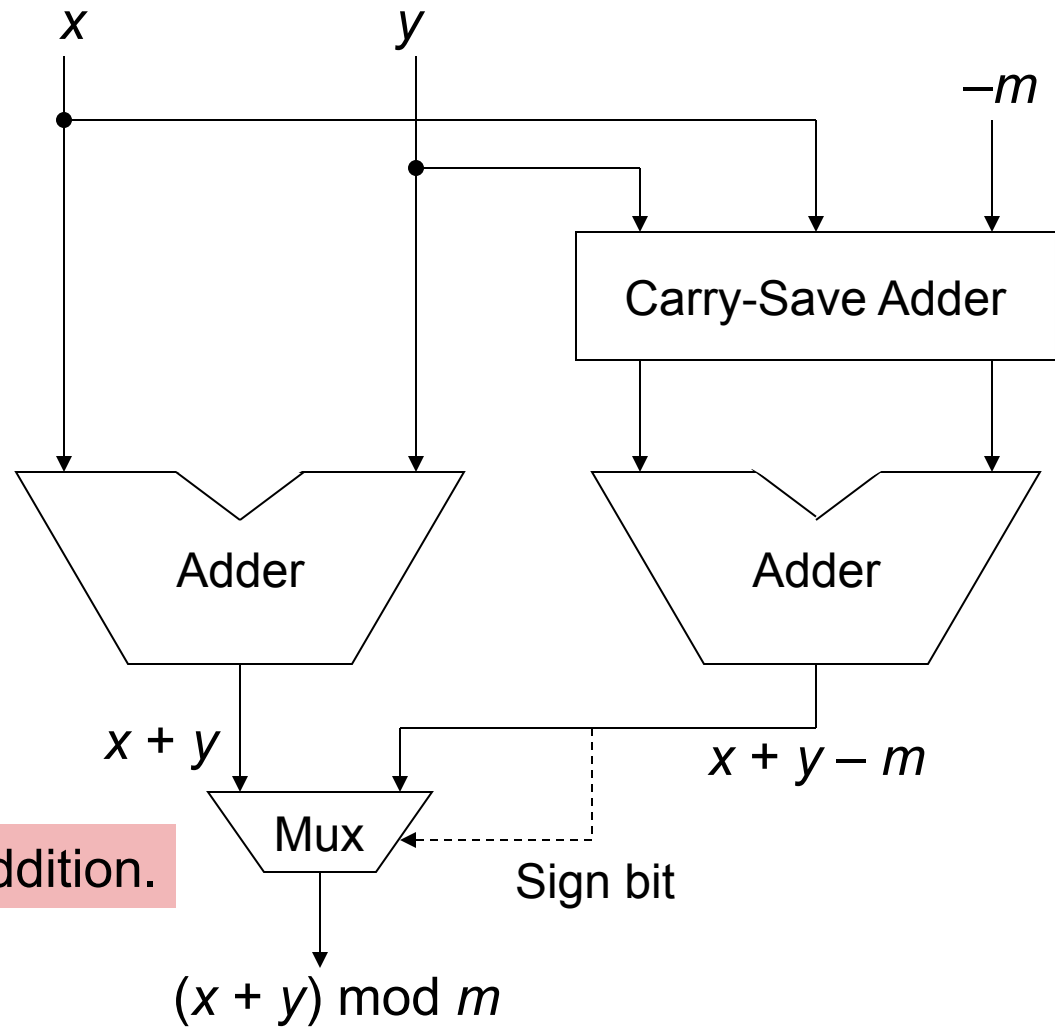


Fig. 7.15 Fast modular addition.

PROBLEMAS

Problema 6.5. Implemente os seguintes somadores modulares:

a) $|A+B|_{29}$.

b) $||A+B|_{27}+C|_{29}$.

c) $||A+B|_{11}+C|_{13}$.

d) $|A+B|_{59}$

e) $|A+B|_{15}$